



Verilog _HDL_Report

**Faculty of Engineering and Technology
Electrical and Computer Engineering Department**

Digital Systems ENCS2340

Name: shaimaa dar taha	ID number:1222440
Section :1	Date:25/1/2024

Instructor: Ismail Khater

الهم ارحم شهداءنا وانصرنا على القوم الظالمين ❤️

Project Description:

In this project, I will design a simple Arithmetic Logic Unit (ALU) using Verilog Hardware Description Language (HDL). The ALU capable of performing four basic arithmetic and logic operations: addition, subtraction, bitwise AND, and bitwise OR.

The Alu take two 4-bit inputs (A and B).


Include a 3-bit control input (OpCode) to select the operation:

- 3'b000: Addition
- 3'b001: Subtraction
- 3'b010: Bitwise AND
- 3'b011: Bitwise OR

Contents:

1. Full adder
2. 4_bit_Adder
3. 4_bit_Subtractor
4. Bitwise AND
5. Bitwise OR
6. Data flow ALU
7. Behavioral_ALU

Full adder :(Fa)

 


A full adder is a fundamental building block in digital electronics used to perform binary addition of three input bits: two single-bit binary numbers (A and B) and a carry-in (C) from a previous stage of addition. It produces two outputs: the sum (Sum) of the three input bits and a carry-out (Cout) that represents whether there is a carry


Verilog code

```
1 module Fa(input a, b, c, output cout, sum);
2   wire w1, w2, w3;
3   // w1: reseve a and b
4   // w2:reseve a xor b
5   //w3: reseve w2 and c
6   // sum=(a xor b)xor c
7   // cout= (a and b)+(a xor b)and c
8   and (w1, a, b);
9   xor (w2, a, b);
10  and (w3, w2, c);
11  xor (sum, w2, c);
12  or (cout, w1, w3);
13  endmodule
14  //shaimaa dar taha
```

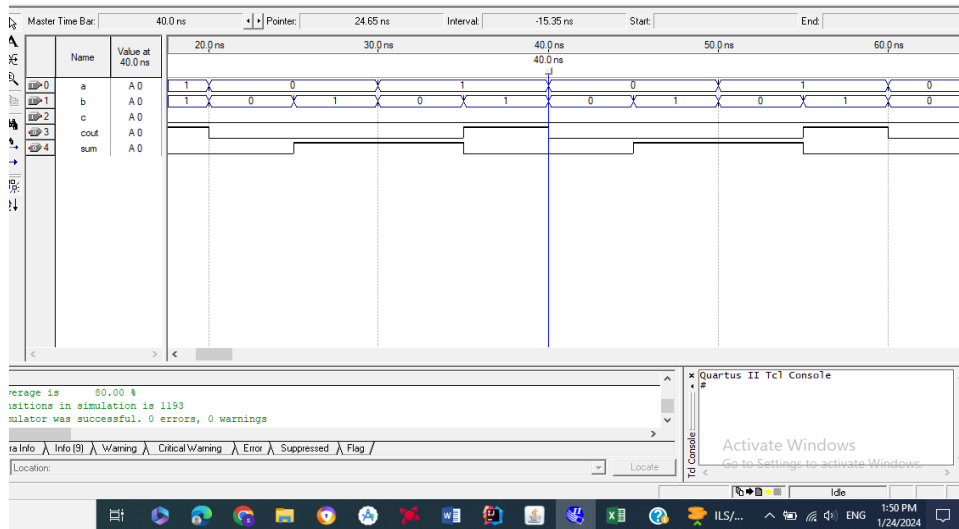Simulation report:(a=0,b=1 ,sum =1,cout =0) so its true



4_bit_Adder :

 


can add two four-bit binary numbers together. It's constructed using four full adders and some additional logic to handle the carry between each stage.


Verilog code :

```
1 module fourBit_adder(input[3:0]a,b,input c,output [3:0]sum,output overFlow,carr);
2 wire [2:0]w;
3 Fa f1( a[0],b[0],c,w[0],sum[0]); // call the module Fa for bit[0]
4
5 Fa f2( a[1],b[1],w[0],w[1] ,sum[1]); // for bit [1]
6
7 Fa f3( a[2],b[2],w[1] ,w[2],sum[2]); // for bit[2]
8
9 Fa f4( a[3],b[3],w[2],carr, sum[3]); // for bit[3]
10
11 xor (overFlow,carr,w[2]); // to find over flow
12
13 //shaimaa dar taha
14 endmodule
15
```

 
Simulation report: (signed number):(3+6= -7 but over flow=1)
,(2+5=7)so the adder work correct



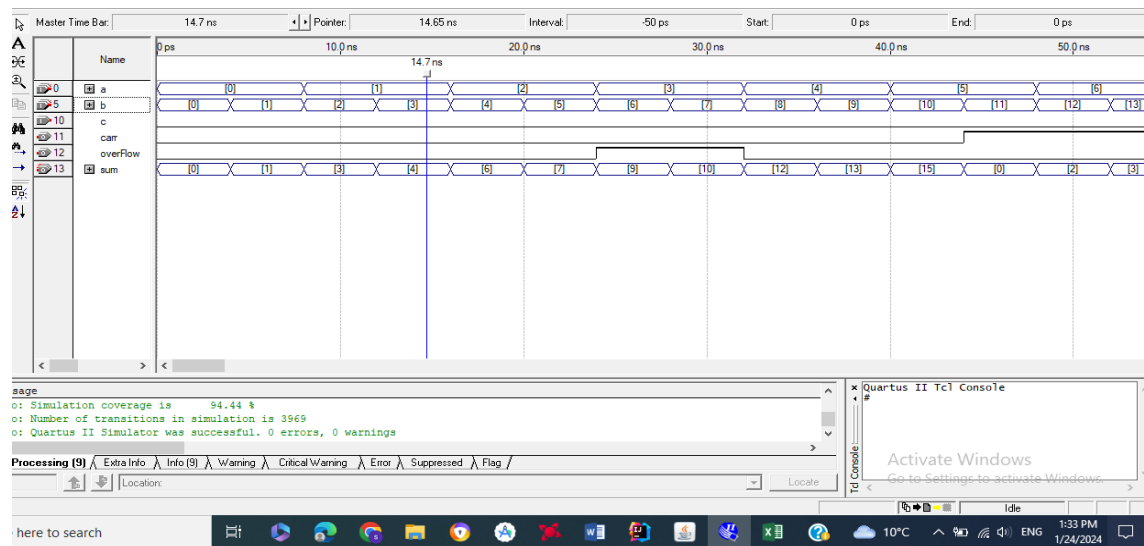ASCII code =the same result at unsigned number :(2+4=6,carry=0)



4_bit_Subtractor

 

four-bit subtractor is a digital circuit that computes the subtraction of two four-bit binary numbers. It's essentially a combination of adders **I call the module (Fa)** and inverters to perform the subtraction operation. One common method to implement a four-bit subtractor is by using a two's complement approach.

Verilog code :

```
1 module four_bit_sub(input[3:0]a,b,input borrow,output[3:0]sub ,output overflow,borrowout);
2   wire [2:0]m;
3   Fa s1( a[0],~b[0],borrow,m[0], sub[0]); // for subtraction bit [0]
4   Fa s2( a[1],~b[1],m[0],m[1],sub[1]); // for subtraction bit [1]
5   Fa s3( a[2],~b[2],m[1],m[2],sub[2]); // for subtraction bit [2]
6   Fa s4( a[3],~b[3],m[2],borrowout,sub[3]); // for subtraction bit [3]
7
8   xor (overflow,borrowout,m[2]); // to find overflow its important when subtract signed number
9
10  // shaimaa Dar taha
11  endmodule
12
```


Another code :

```


1  module four_bit_sub(input[3:0]a,b,input borrow,output[3:0]sub ,output overFlow,borrowout);
2  wire [2:0]m;
3  wire[3:0]nb;
4  not g1(nb[0],b[0]);
5  not g2(nb[1],b[1]);
6  not g3(nb[2],b[2]);
7  not g4(nb[3],b[3]);
8
9
10 Fa s1( a[0],nb[0],borrow,m[0], sub[0]); // for subtraction bit [0]
11 Fa s2( a[1],nb[1],m[0],m[1],sub[1]); // for subtraction bit [1]
12 Fa s3( a[2],nb[2],m[1],m[2],sub[2]); // for subtraction bit [2]
13 Fa s4( a[3],nb[3],m[2],borrowout,sub[3]); // for subtraction bit [3]
14
15 xor (overFlow,borrowout,m[2]); // to fined over flow its imporent when subtract signed number
16
17 // shaimaa Dar taha
18 endmodule
19

```

 
Simulation report: (signed number): (3-6=-3 ,over flow =0)so the module is correct



 Simulation report: (unsigned number):(5-10=11 but over flow is 1)




Bitwise AND:

 


Verilog code : this module all 4 bit(a)anding with 4 bit (b)

```
1 module AndGate(input [3:0]a,b,output [3:0]And);
2 //and gate for every bit in a with every bit in b
3
4 and(And[0],a[0],b[0]);
5 and(And[1],a[1],b[1]);
6 and(And[2],a[2],b[2]);
7 and(And[3],a[3],b[3]);
8 //shaimaa Dar taha
9 endmodule
```

 Simulation report: (0000 and 0000 give 0000)so the simulation is true



 Bitwise OR: Verilog code : this module all 4 bit(a) oring with 4 bit (b)





```


1 module OrGate(input[3:0]a,b,output [3:0] Or);
2 // take 2 number with 4 bit and oring them
3 or(Or[0],a[0],b[0]);
4 or(Or[1],a[1],b[1]);
5 or(Or[2],a[2],b[2]);
6 or(Or[3],a[3],b[3]);
7 // shaimaa dar taha
8 endmodule
9

```

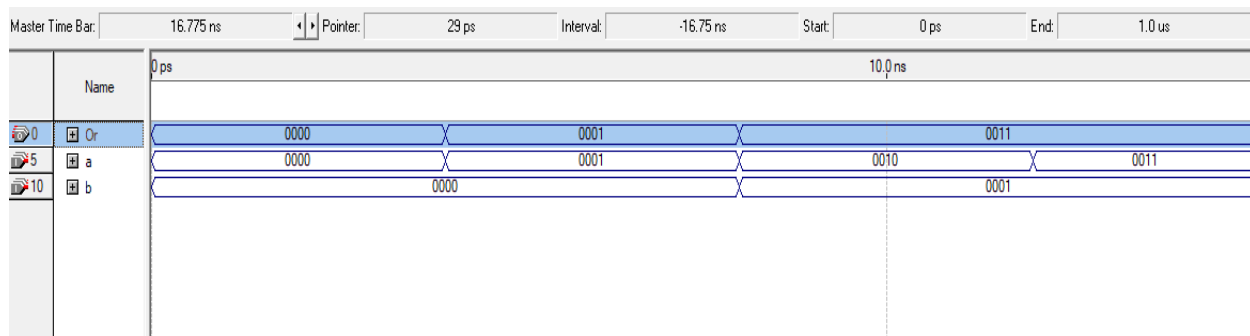Simulation report: (0000 or 0001 = 0001) so the simulation is true



Data flow ALU:

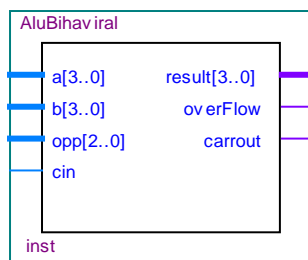

Module for ALU that capable of performing four basic arithmetic and logic operations: addition, subtraction, bitwise AND, and bitwise OR.in data flow

Verilog code:

```

1 module AluDataflow(output [3:0]Result,output overflow,Carry,input[3:0]a,b,input cin,input[2:0]opp);
2   wire [3:0]add,sub,andBitwise,orBitwise; //for the result
3   wire carr1,carr2,overflow1,overflow2; // for carry and over flow
4
5
6   fourBit_adder k1(a,b,cin,add,overflow1,carr1);
7
8   four_bit_sub k2(a,b,cin,sub,overflow2,carr2);
9
10  OrGate k3(a,b, orBitwise);
11
12  AndGate k4(a,b,andBitwise);
13
14  assign Result =(opp==3'b000)?add: // to assign the result for the ALU depends on opp code
15    (opp==3'b001)?sub:
16    (opp==3'b010)?andBitwise:
17    (opp==3'b011)?orBitwise:
18    3'bz; // dont care if op =4,5,6,7
19
20  assign overflow =(opp==3'b000)?overflow1: // to assign the over flow for the subtraction and addition only
21    (opp==3'b001)?overflow2:
22    3'bz;// dont care if opp 2,3,4,5,6,7
23
24  assign Carry =(opp==3'b000)?carr1:// to assign the carry for the subtraction and addition only
25    (opp==3'b001)?carr2:
26    3'bz; // dont care
27    // shaimaa dar taha
28  endmodule
29

```


Simulation report: (signed number)

when opp=000 (add)(0+1=1) carry is 0 ,over flow is 0 **its true**


when opp=001(sub)(2-4= -2)so **its true**

When opp=010(and)(0011&0110=0010) **its true**

When opp =011(or)(0100| 1001=1101=-3)so **its true**

 

Simulation report: (unsigned number):

 

Behavioral_ALU:

Module for ALU that capable of performing four basic arithmetic and logic operations: addition, subtraction, bitwise AND, and bitwise OR.in behavioral

Verilog code:

```


1  module AluBihaviral(input [3:0]a,b,input [2:0]opp,input cin ,output reg [3:0]result ,output reg overFlow,carrou);
2
3  wire [3:0]add,sub,andBitwise,orBitwise ; //for the result
4  wire carr1,carr2,overflow1,overflow2; // for carry and over flow
5
6
7  fourBit_adder k1(a,b,cin,add,overflow1,carr1);
8  four_bit_sub k2(a,b,cin,sub,overflow2,carr2);
9  OrGate k3(a,b, orBitwise);
10 AndGate k4(a,b,andBitwise);
11
12 // always @(a,b,opp,cin)
13 always @(*)
14 begin
15 if (opp==3'b000) result =add;
16 else if (opp==3'b001) result=sub ;
17 else if (opp==3'b010) result= andBitwise;
18 else if (opp==3'b011) result=orBitwise ;
19 else result =4'bz;
20 // end of result
21 if (opp==3'b000) carrout=carr1;
22 else if (opp==3'b001) carrout=carr2;
23 else carrout=1'bz;
24 //end of carry
25 if (opp==3'b000) overFlow=overflow1;
26 else if (opp==3'b001) overFlow=overflow2;
27 else overFlow=1'bz;
28 end
29 endmodule
30

```


Simulation report: (signed number) (true 3-6=-3, 0+1=1)



Simulation report: (unsigned number):

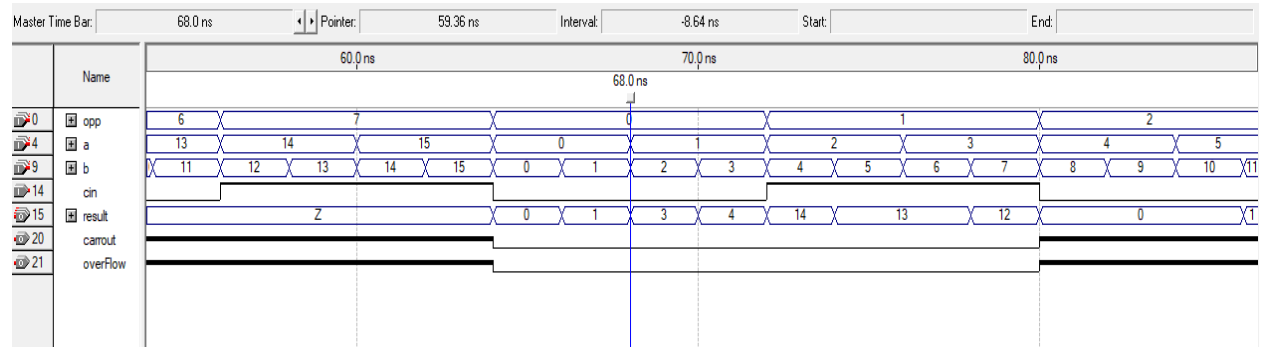

Sympole for project:

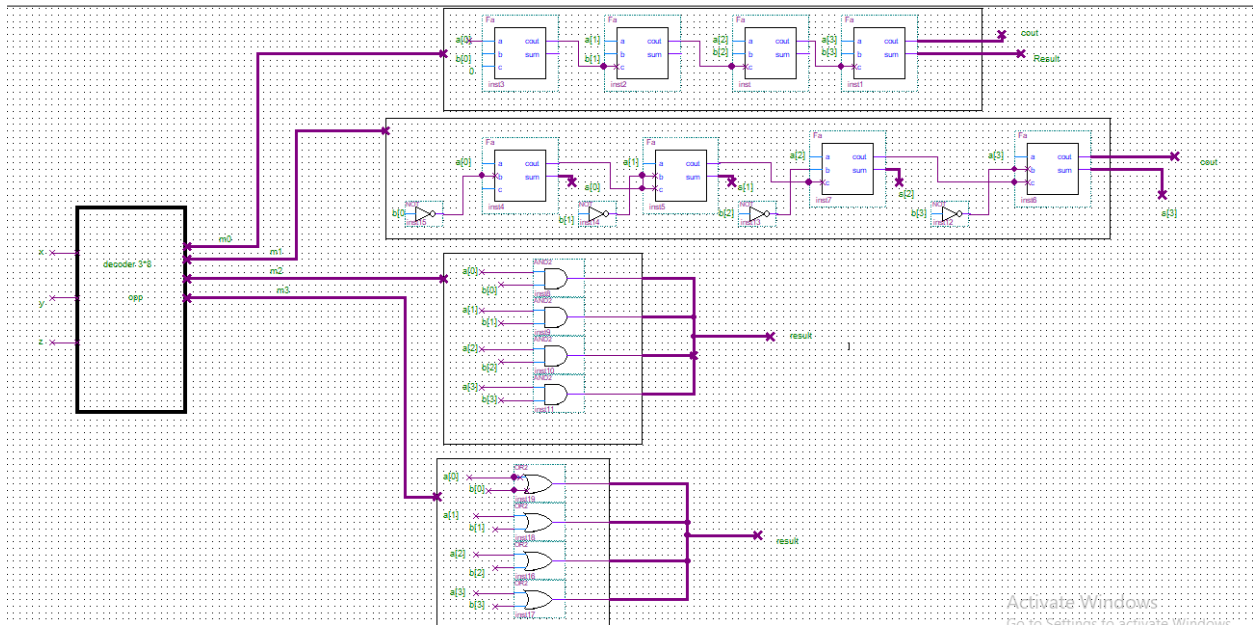

Another sympole:

